

# Super-cap Stay Alive

by

Jamie Robinson




# What is “Stay-Alive”?

- With DC locomotives, a smooth mechanism and addition of a flywheel would typically move a loco through minor electrical interruptions
- DCC-equipped locomotives, especially when sound-equipped, are far more prone to electrical interruption with resultant jerking and performance changes depending on what type of decoder it is equipped with
- A stay-alive unit is a capacitor that stores a small amount of electricity to power the loco and maintain sound integrity for a brief interval

Stay-alive units are available from several manufacturers, for example:


**ESU Loksound Power Pack**

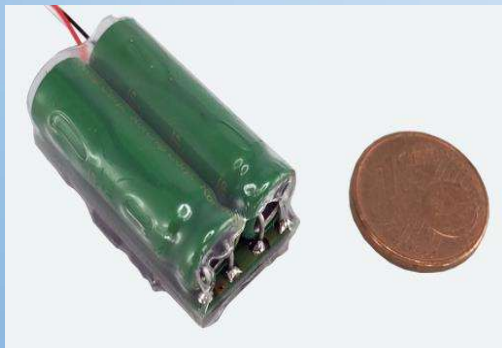

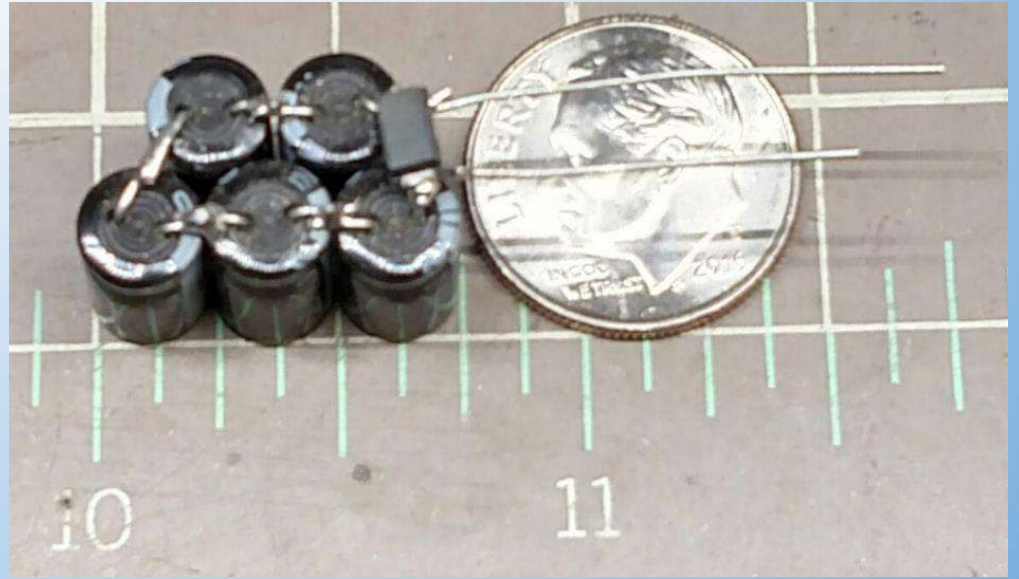**TCS Keep Alive**





- Pre-packaged stay-alive units may not fit into your specific loco easily, and can be pricey...
- With the decreasing size of so-called “super” capacitors, it is now feasible to build small customized stay-alive units to fit almost any locomotive, and it’s very inexpensive!
- By purchasing the capacitors in lots of 100, cost per stay-alive unit is less than \$5.00
- This presentation will demonstrate some of the possibilities



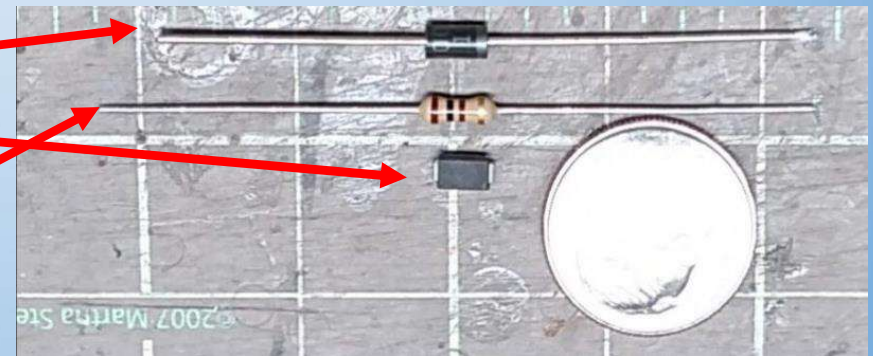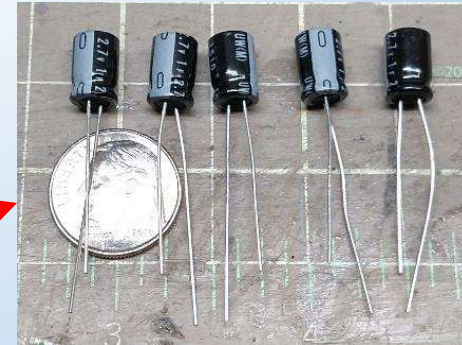
# You will need the following components

- C1 - C5      2.7v 1F capacitors
- D1            1N4001 (or similar) diode
- D2            13v 1.5w Zener diode
- R1            100 ohm  $\frac{1}{4}$  or  $\frac{1}{2}$  watt resistor




Here's the circuit diagram

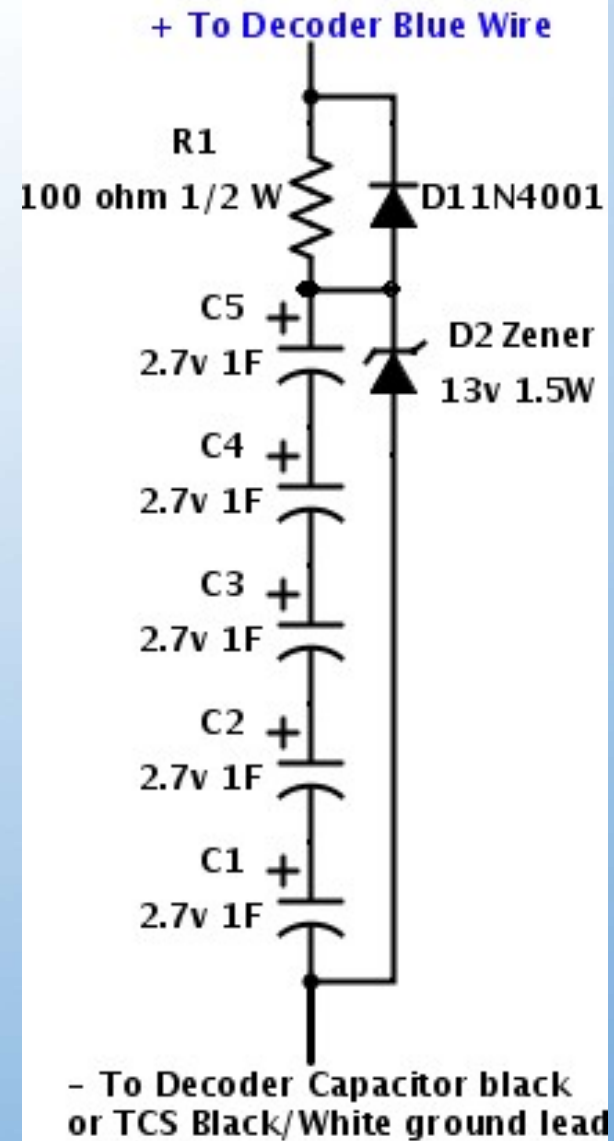
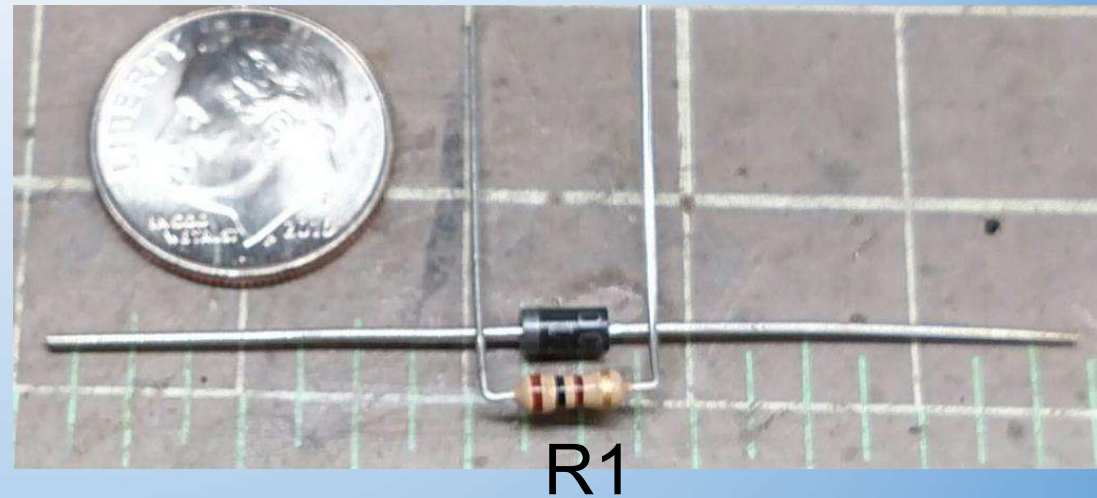
# Limiting Inrush Current


- We use D1 and R1 to limit the rate of charge to prevent circuit breakers from tripping
- R1 is a 100 ohm  $\frac{1}{4}$  (or  $\frac{1}{2}$ ) watt resistor




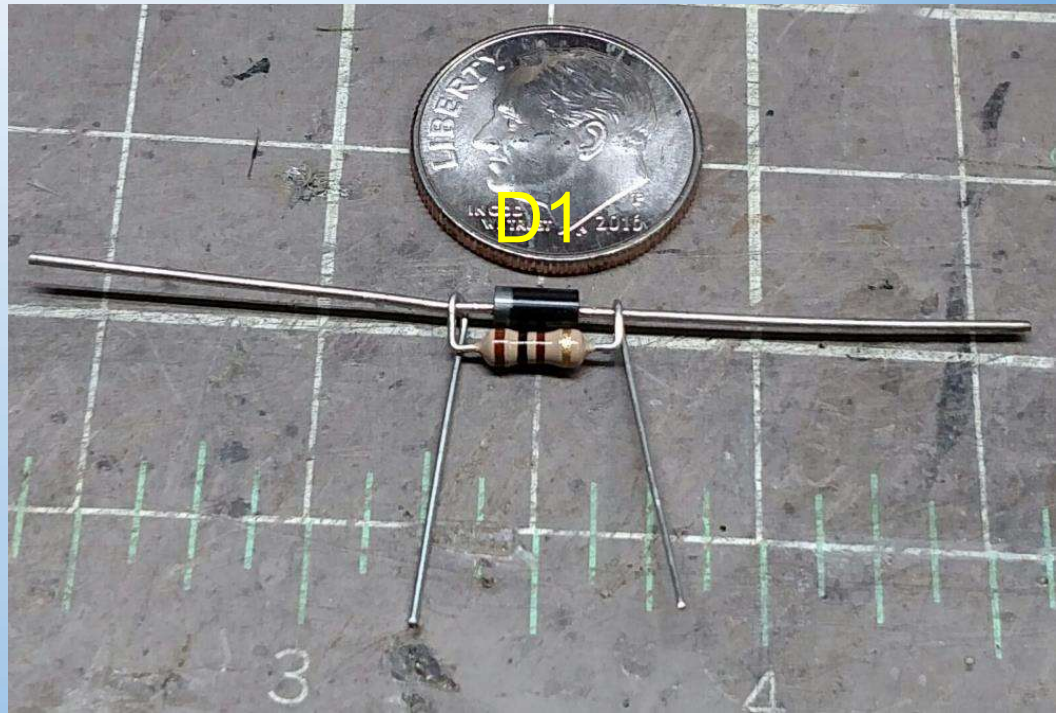
# Limiting Inrush Current


- We use D1 and R1 to limit the rate of charge to prevent circuit breakers from tripping
- R1 is a 100 ohm  $\frac{1}{4}$  (or  $\frac{1}{2}$ ) watt resistor
- Diode D1 prevents the flow of electricity in one direction




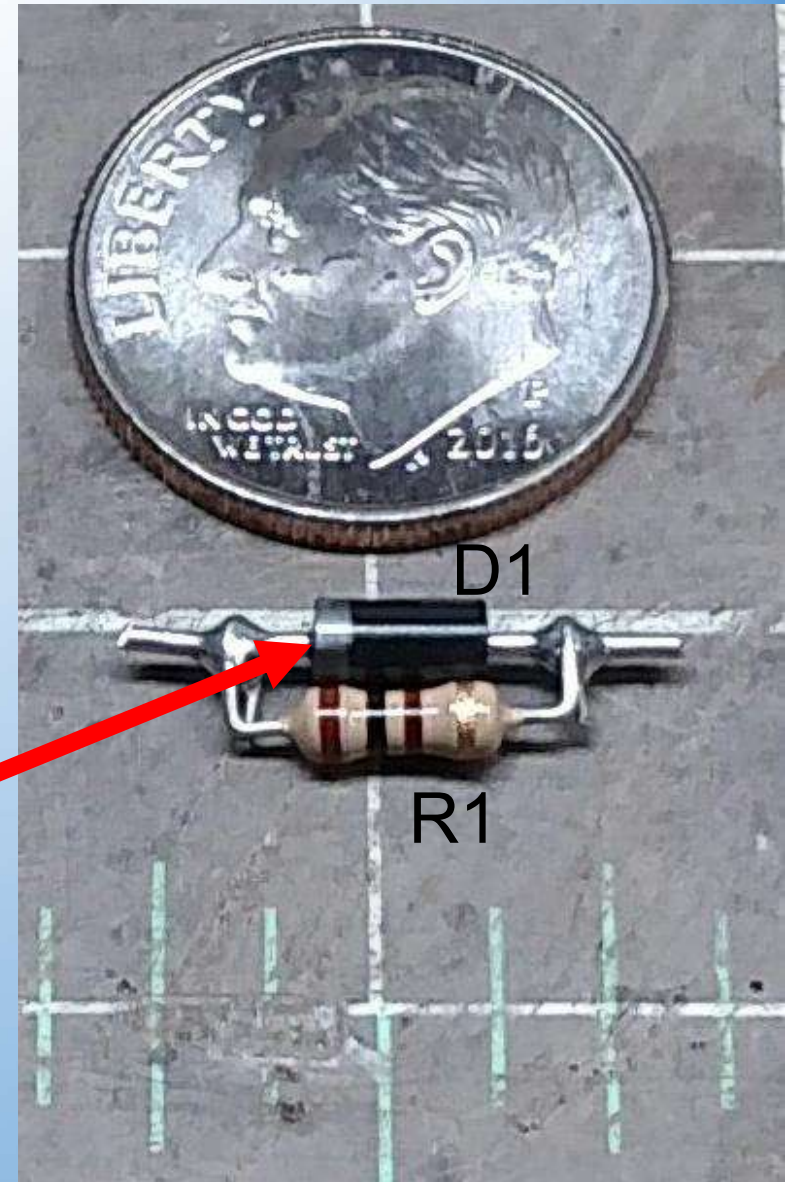
# Limiting Inrush Current

- We use D1 and R1 to limit the rate of charge to prevent circuit breakers from tripping
- R1 is a 100 ohm  $\frac{1}{4}$  (or  $\frac{1}{2}$ ) watt resistor
- Diode D1 prevents the flow of electricity in one direction
- D1 has a silver band on one end; that is the positive (+) end




# We use a Zener diode to limit maximum voltage to the capacitors

- D2 is a 13 volt 1.5 watt Zener diode
- It limits the capacitor voltage to 13 volts
- **This is extremely important** – capacitors can explode if exposed to excessive voltage
- This is the banded (+) end (it can be hard to see)


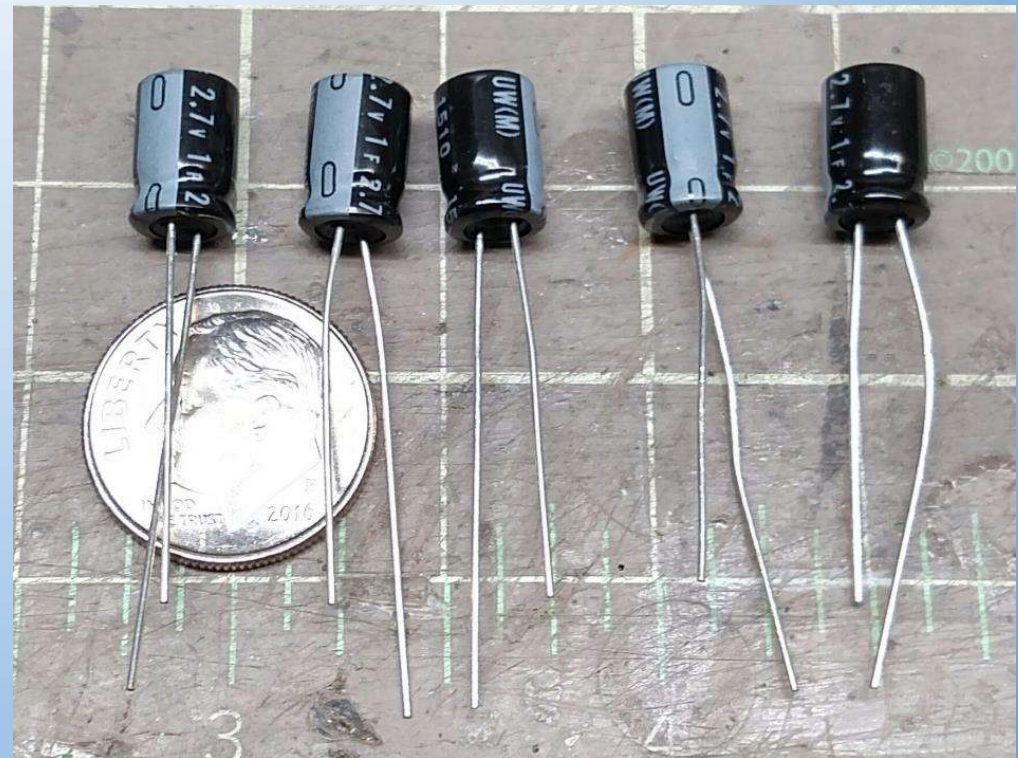
# Capacitors


- C1 – C5 are 2.7 volt 1 Farad capacitors
- They store the electricity and act like small batteries
- Most capacitors are polarity-sensitive; the negative (-) lead is the short one and is marked on the case
- When capacitors are connected in series, their voltage is additive, so the max voltage is  $2.7 \times 5 = 13.5$  volts
- Capacitance divides in series though, so total capacitance here is  $1\text{F} / 5 = .2\text{ F}$  or 200,000 micro-farads





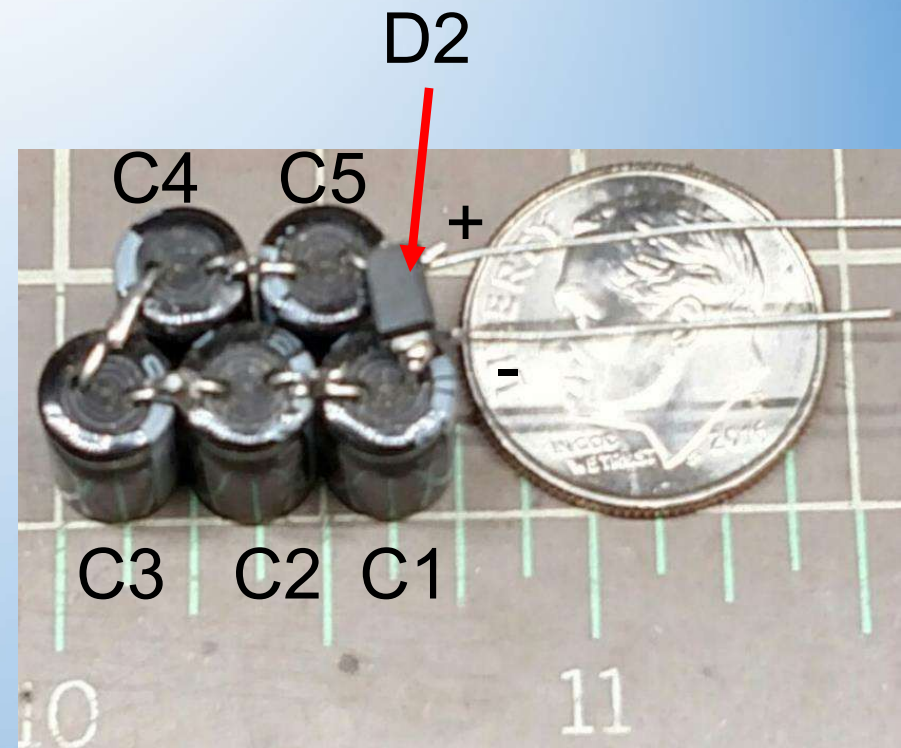
# Wire it up

- Here's an easy configuration
- The 5 caps are soldered in series
- D2 is soldered across the + and - leads



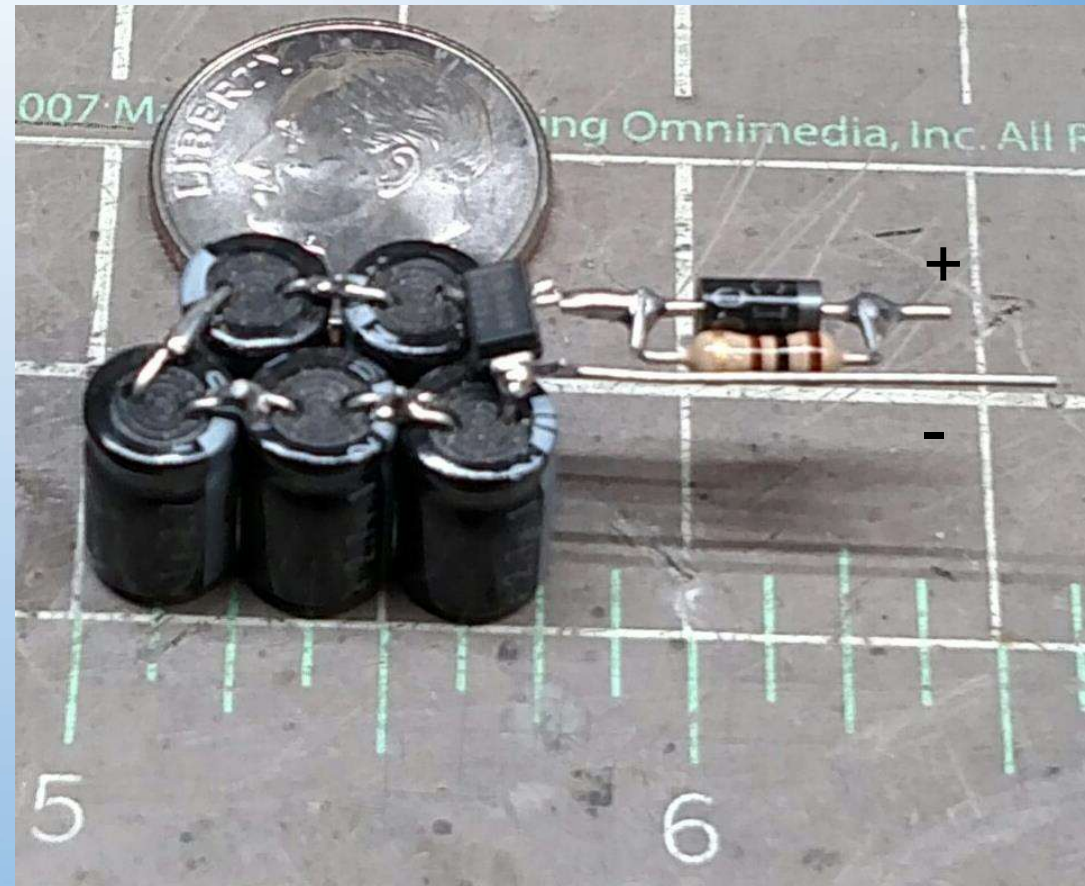
# Add the Inrush Limiter

- We add the Inrush Limiter to the Positive lead, with the silver band of D1 pointed out
- Now we have two leads to be attached to the decoder
- The positive lead is attached to the decoder blue wire
- You may need to do some investigating to see where to attach the negative lead


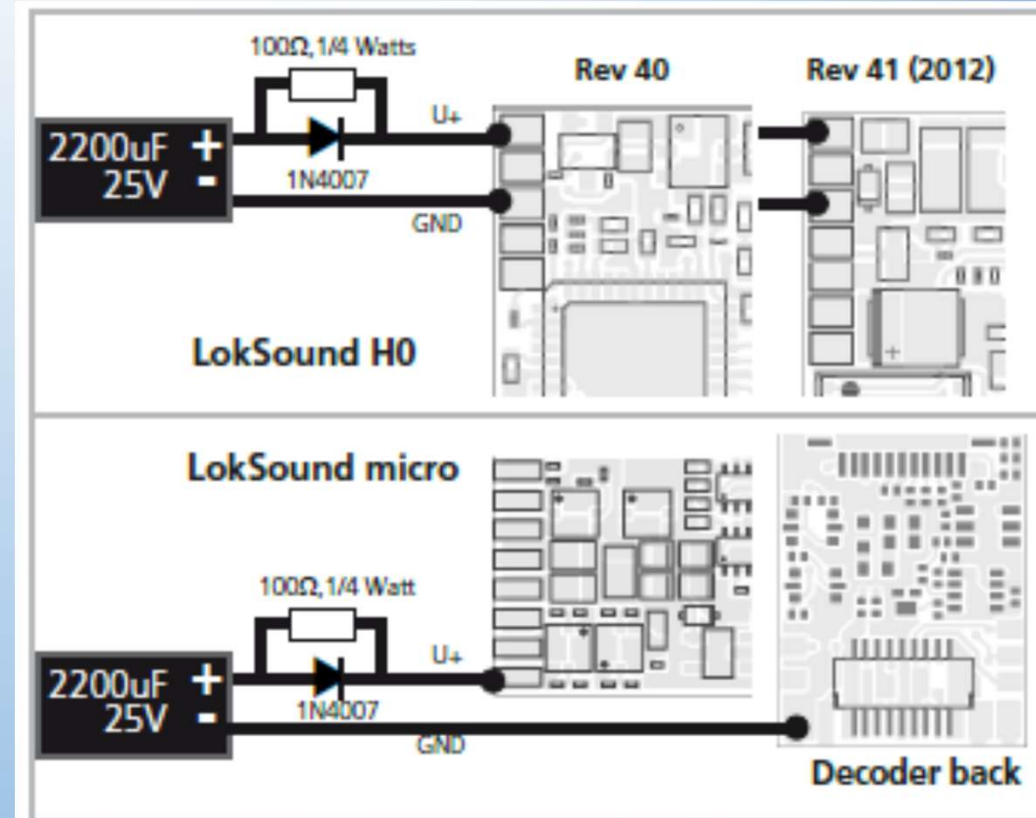
# Hooking It Up


- On TCS decoders, attach the negative lead to the black and white “ground” lead
- On Tsunami decoders, attach it to the capacitor black lead
- On Loksound 4.0 decoders, attach it to the board as shown in the manual






# Sample Installations

**In a coach on perf-board**

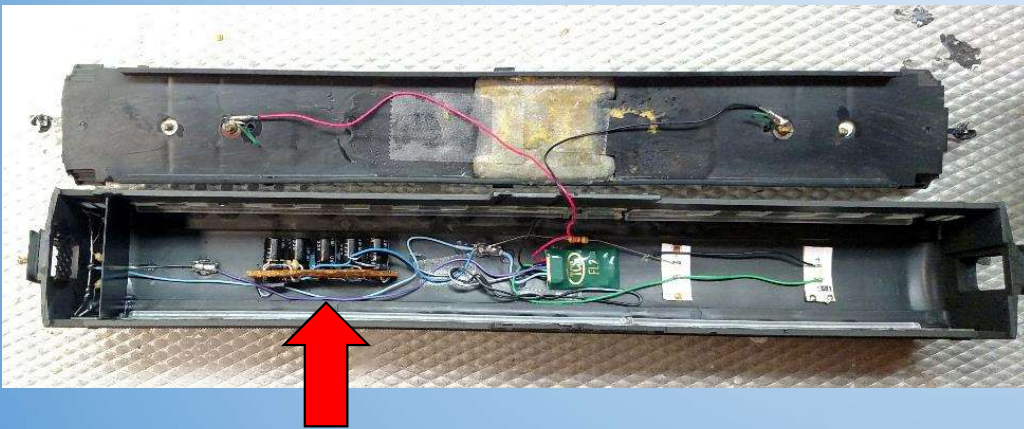


**Atlas RS-1 – caps split up**

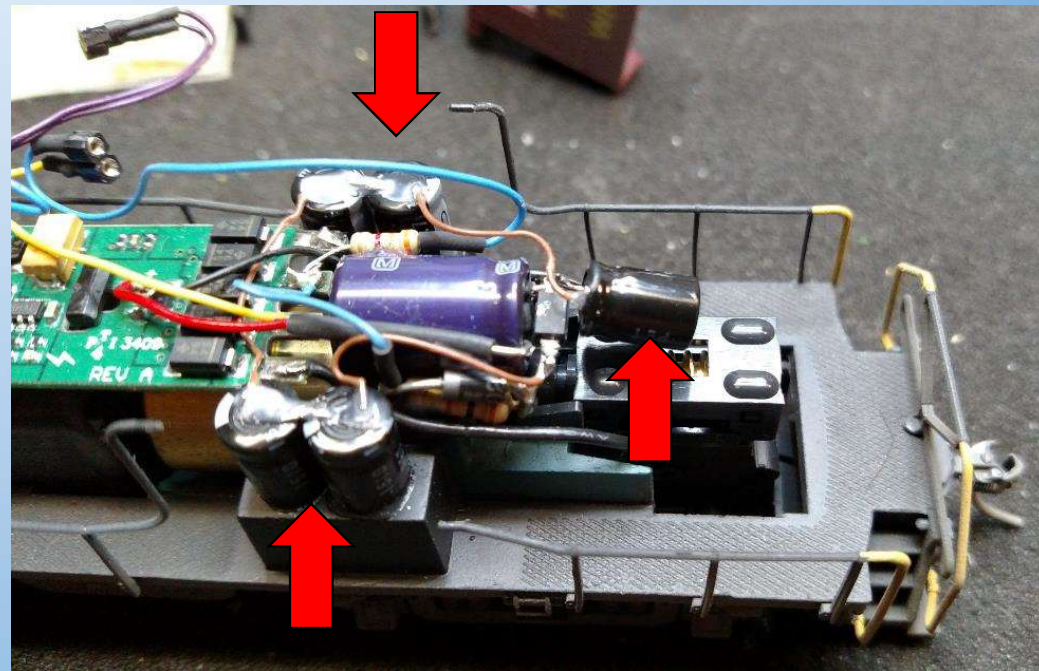


# Sample Installations

**Model Power E-8**

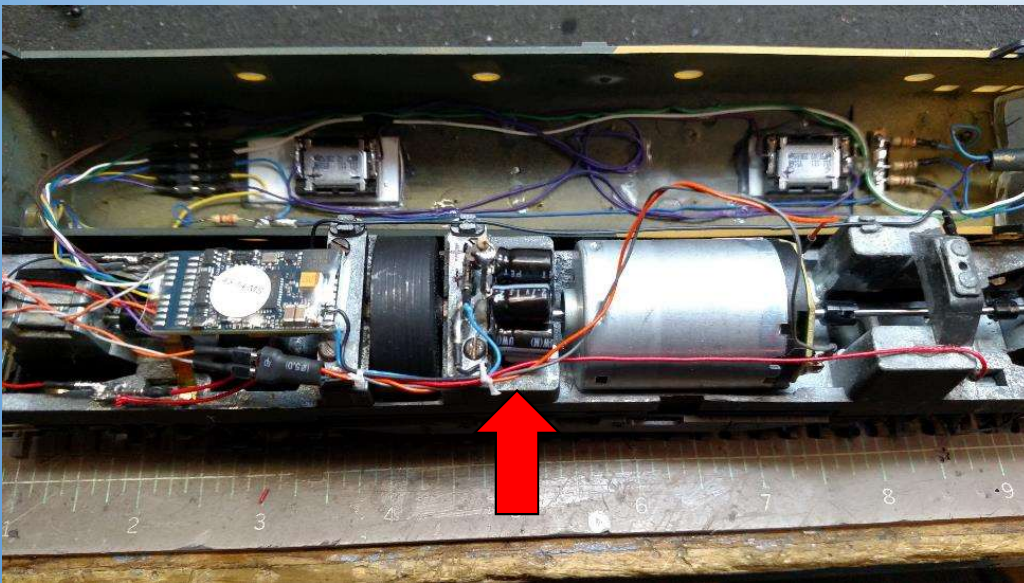

**Athearn U-33C – caps split up**

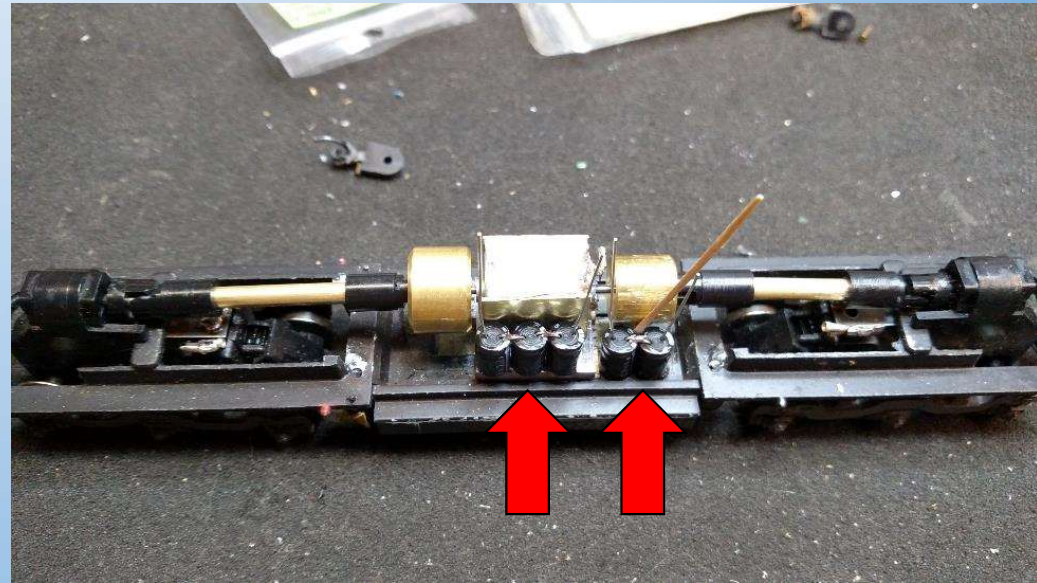




# Sample Installations

**Model Power FB-2**



**Model Power FA-2 – caps split up**

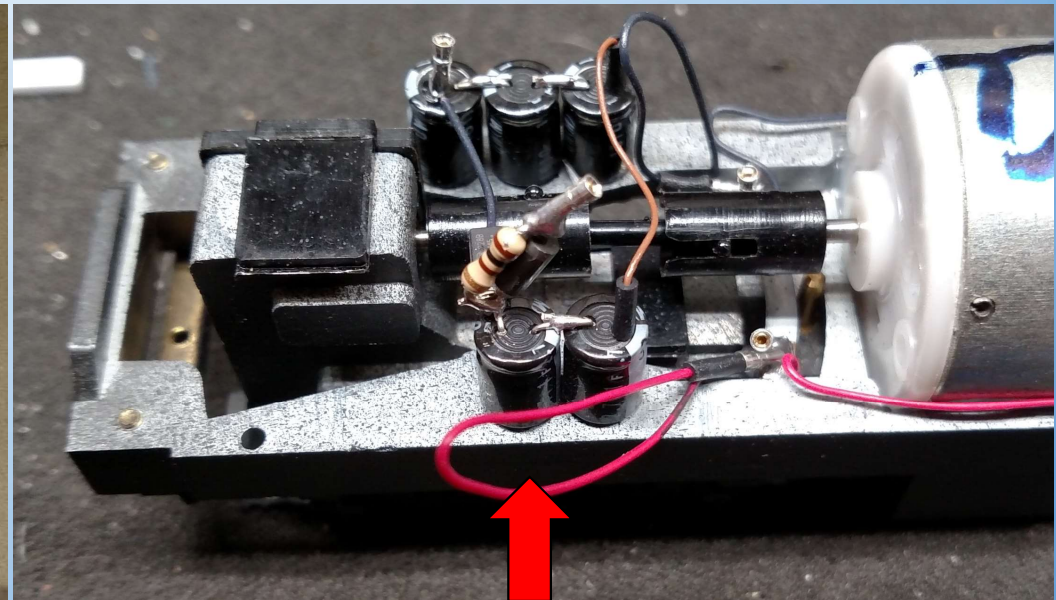

# Just Remember

- There's still no substitute for a smooth mechanism
- Don't be afraid to add pick-up wipers – don't rely on rotating equipment to provide good electrical contact
- Consider using dead blocks to protect lift-out or swing-out layout sections
- Once a loco is on stay-alive, you no longer have control – there's such a thing as too much!
- There's a handout with a parts list and supplier info, as well as some supporting web links
- Enjoy! Build a couple – they will help your sound units

# Parts

- <http://www.mouser.com/>
- 647-JUWT1105MCD Super Capacitors (C1 – C5)
- 512-1N4001 Diode (D1)
- 863-1SMA5928BT3G Zener Diodes (D2)
- 279-CFR50J100R Resistor (R1)

# Web Links

- <http://www.members.optusnet.com.au/mainnorth/alive.htm>
- <http://wayback.archive.org/web/20120729061658/http://www.members.optusnet.com.au/mainnorth/alive.htm>